


Protection for Field Transmitters: Requirements, Challenges, Solutions

Vito Shen
Sep 2017


Agenda

- Introduction to IEC61000-4 EMC Immunity Test Suite
- Surge Protection with TVS Diode and implications for the system
- Example Implementation 1: Loop-powered 4-20mA Transmitter
- Example implementation 2: Combined Voltage / Current output

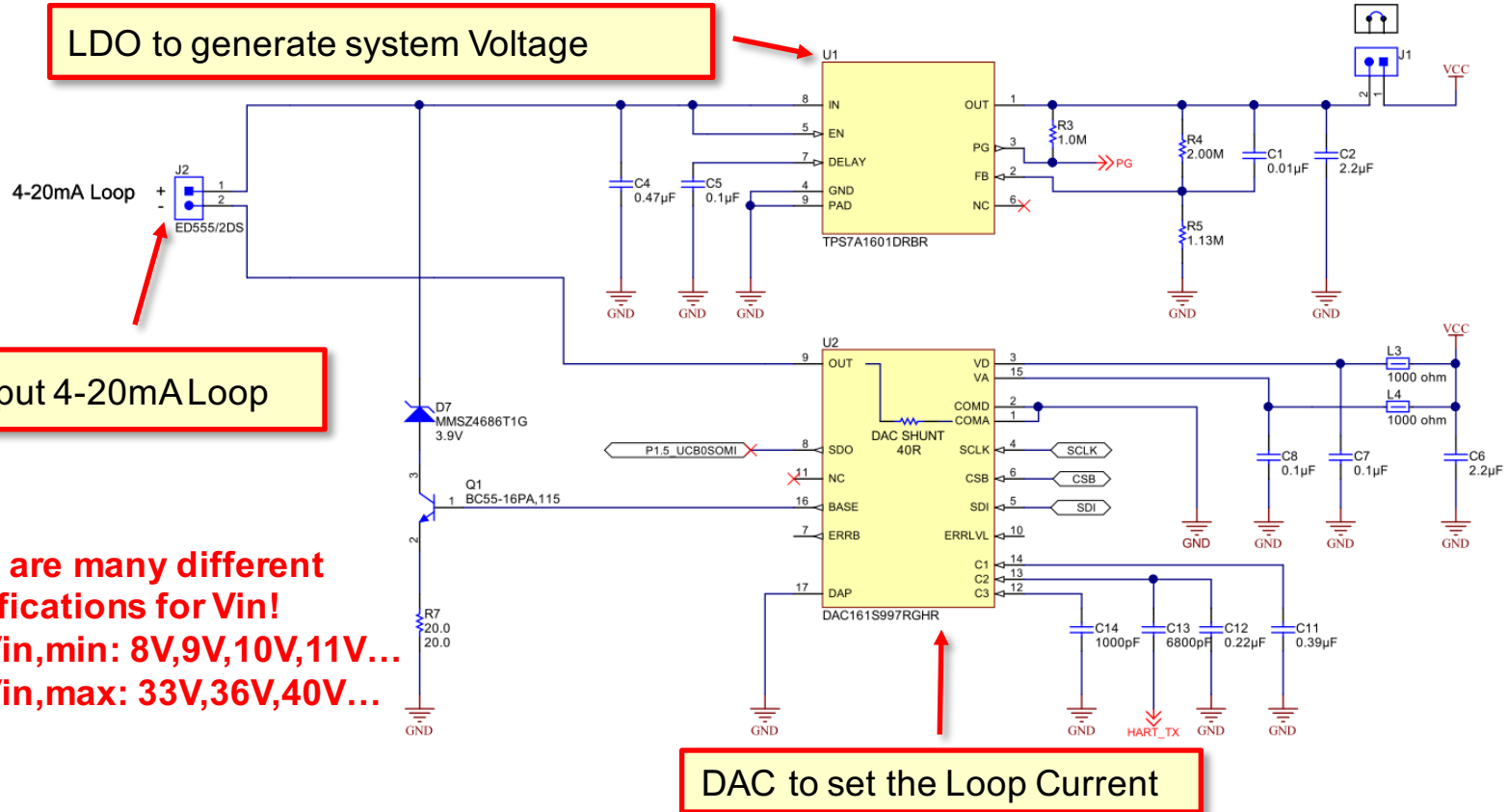Simplified circuit of loop powered 4-20mA Sensor



Did you promote the correct solution...

 


© Kevin Duke

Catastrophic board failure during SURGE test


IEC61000-4 EMC Immunity Test Standards

 IEC61000-4 contains 35 different immunity test standards






Most commonly applied immunity tests:

- **Electrostatic Discharges**
 - IEC61000-4-2: Electrostatic Discharge Immunity
- **HF Conducted Disturbances**
 - IEC61000-4-4: Electrically Fast Transient Immunity
 - **IEC61000-4-5: Surge Immunity**
 - IEC61000-4-6: Conducted Immunity Tests
- **HF Radiated Disturbances**
 - IEC61000-4-3: Radiated Immunity
 - IEC61000-4-9: Pulse Magnetic Field Tests
- **LF Radiated Disturbances**
 - IEC61000-4-8: Power Frequency Magnetic Field Immunity



 


   Comparison of pulse power and pulse energy



Source: Datasheet; SN65HVD7x 3.3-V Supply
RS-485 With IEC ESD Protection; [sllse11d](#)

Example Test Setup

  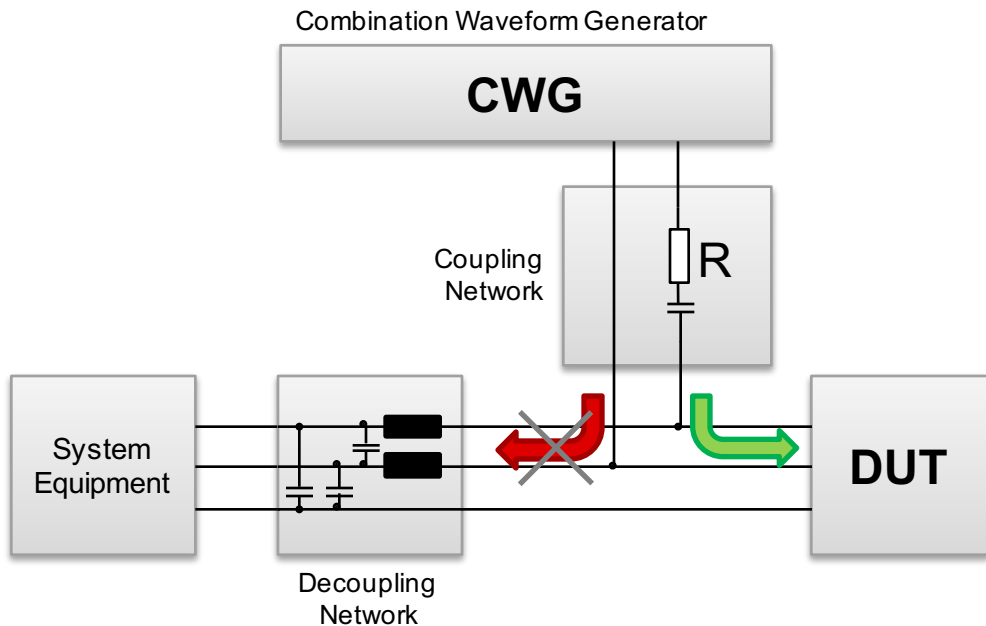

EFT and Surge waveform equations and simulation models

https://e2e.ti.com/support/interface/industrial_interface/m/videos_files/665146/download

Voltage Levels, CN & Max Peak Currents

| Level | Open Circuit Test Voltage [kV] | Description | Maximum Peak Current [A] | | |
|-------|--------------------------------|--|--------------------------|-------|------|
| | | | R=42Ω | R=12Ω | R=2Ω |
| 1 | 0.5 | Partly protected electrical environment | 12 | 42 | 250 |
| 2 | 1 | Electrical environment where the cables are well-separated, even at short runs | 24 | 84 | 500 |
| 3 | 2 | Electrical environment where cables run in parallel | 48 | 167 | 1000 |
| 4 | 4 | Electrical environment where the interconnections are run as outdoor cables along with power cables, and the cables are used for both electronic and electric circuits | 96 | 334 | 2000 |
| X | Custom | Special conditions specified in the product specification | x | x | x |


- Usually the dedicated product standard specifies the specific test conditions.
- Transmitter applications require most often to test with 1 kV / 42 Ω common mode, customers apply even differential mode

Source: App Report; IEC 61000-4-x Tests for TI's Protection Devices; [slva711](#)

8

Performance Criteria for Surge (IEC 61000-4-5)

| Performance Criteria | Description |
|----------------------|--|
| A | Performance within specification limits |
| B | Temporary degradation which is self-recoverable |
| C | Temporary degradation which requires operator intervention |
| D | Loss of function which is not recoverable |

 

Which performance criteria is met?

How can the system be protected?


Examples:

- Transient Voltage Suppressor (TVS) Diode
- Gas Discharge Tube (GDT)
- Steering Diodes
- Current limiting circuitry
- Combination of the above mentioned


Agenda

- Introduction to IEC61000-4 EMC Immunity Test Suite
- Surge Protection with TVS Diode and implications for the system
- Example Implementation 1: Loop-powered 4-20mA Transmitter
- Example implementation 2: Combined Voltage / Current output


Transient Voltage Suppressor (TVS) Diode

 

  
 
| Symbol | Parameter |
|---------------|-------------------------------------|
| V_R, V_{RM} | Stand-off voltage |
| I_R, I_{RM} | Reverse Leakage @ V_R |
| V_{BR} | Breakdown voltage @ I_{BR} & T |
| I_{BR}, I_T | Breakdown Current |
| αT | Temperature Coefficient of V_{BR} |
| V_C, V_{CL} | Clamping voltage @ I_{PP} |
| I_{PP} | Peak pulse current |
| R_D | Dynamic resistance |
| $P_{PP(M)}$ | (Max) Peak pulse power |
| $V_{F(M)}$ | (Peak) Forward voltage drop |
| $I_{F(M)}$ | (Peak) Forward current |






Transient Voltage Suppressor (TVS) Diode



 No continuous operation at those conditions !!!





TVS – Standard series
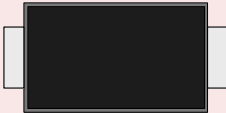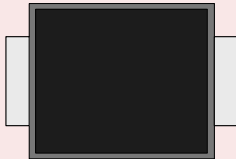 
| | SMAJ | SMBJ | SMCJ | SMLJ SMDJ |
|--------------------|---|---|---|-----------------------|
| Peak Pulse Power * | 400W | 600W | 1500W | 3000W |
| Package |  <p>SMA DO-214AC</p> |  <p>SMB DO-214AA</p> |  <p>SMC DO-214AB</p> | |
| Package Size | 5.2 x 2.6 mm ² | 5.4 x 3.6 mm ² | 7.9 x 5.9 mm ² | |
| Package Area | 13.52 mm ² | 19.44 mm ² | 46.61 mm ² | |
| Pad Size | 5 x 5 mm ² | | | 8 x 8 mm ² |

* For 10/1000μs pulse

TVS - Basic Simulation

 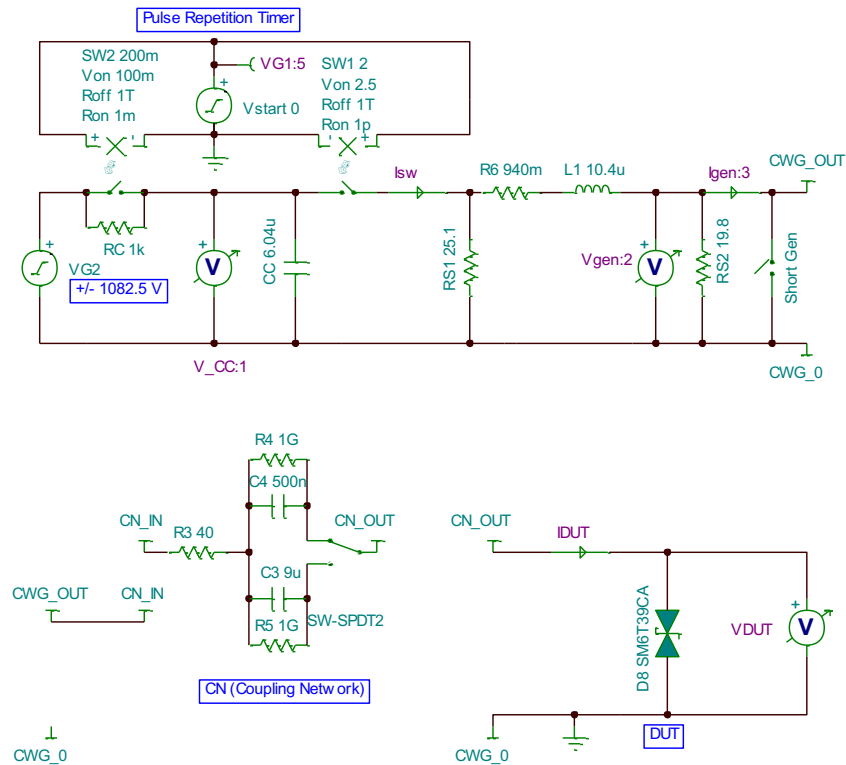CWG (Combination Wave Generator) - $R_i = 2 \text{ Ohm}$




Current

Voltage

Any single surge current pulse leads to a positive / negative voltage pulse

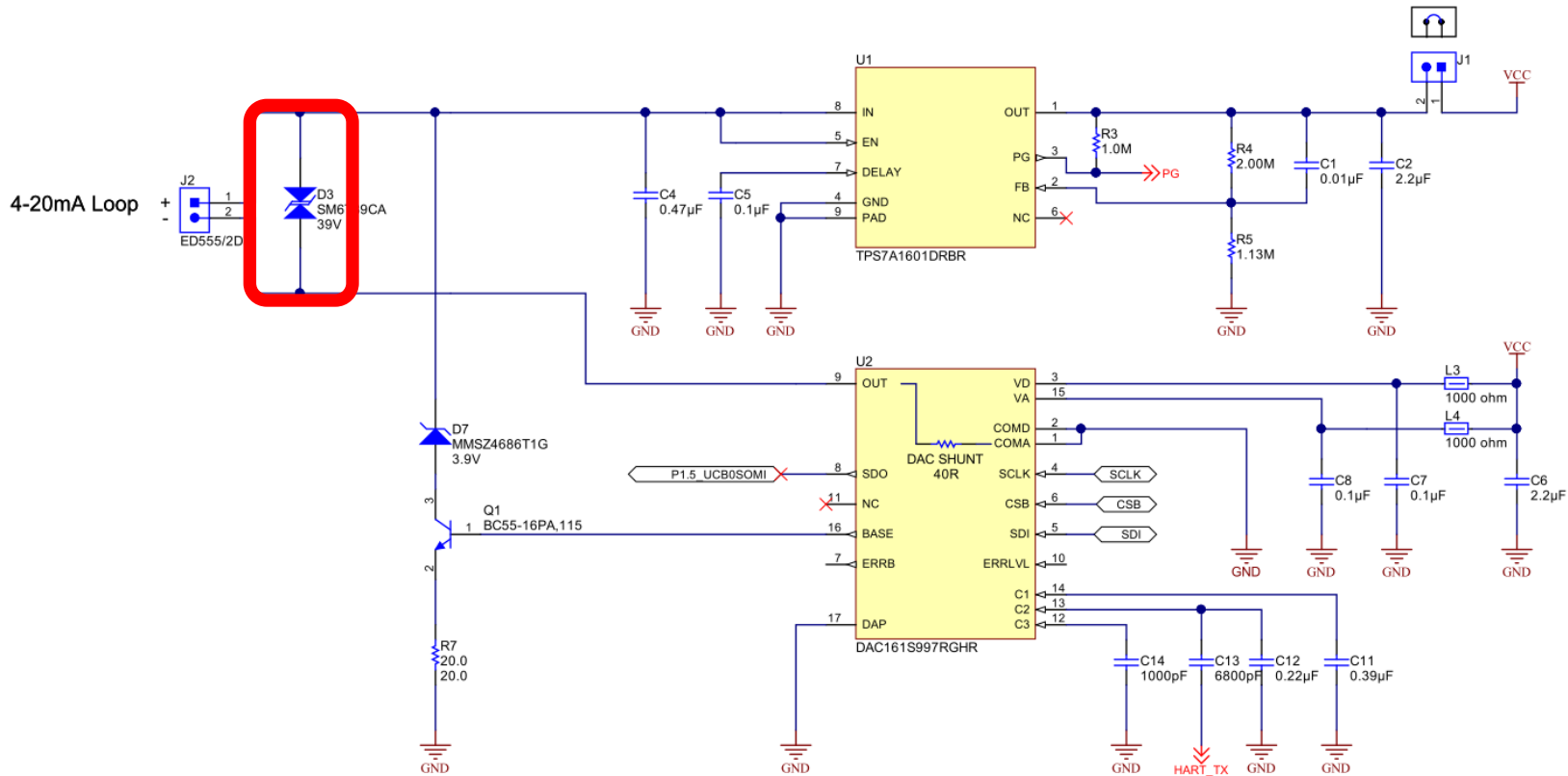Modified Schematic with TVS Diode at the Input



Example: TVS Diode Calculation

$$P_{PP} = V_{CL} \times I_{PP} = 53.3V \times 11.3A = 602.3W @ 25^{\circ}C; 10/1000\mu s$$

Peak Pulse Power for 20 μ s from graph: 3.5kW **Not accurate**

From Temperature Derating graph (@125 $^{\circ}$ C): 3.5kW \times 70 % = 2.45kW

$$R_D = \frac{V_{CL} - V_{BRmax}}{I_{PP}} = \frac{53.3V - 40.6V}{11.3A} = 1.124\Omega \quad \text{Only valid for 10/1000}\mu s \text{ pulse}$$

$$V_{CL@25^{\circ}C} = R_D \times I_{PP} + V_{BRmax} = 1.124\Omega \times 24A + 40.6V = 67.6V$$


$$P_{PP} = V_{CL} \times I_{PP} = 67.6V \times 24A = 1.62kW @ 25^{\circ}C \quad \rightarrow \text{1.78kW@125}^{\circ}C$$

$$V_{CL@125^{\circ}C} = V_{CL@25^{\circ}C} \times (1 + \alpha T \times (T - 25)); \alpha T = 0.1\%/^{\circ}C \text{ (typical)}$$

$$V_{CL@125^{\circ}C} = V_{CL@25^{\circ}C} \times (1 + 0.001 \times 100) = 67.6V \times 1.1 = 74.36V$$

Modified Schematic with TVS Diode at the Input

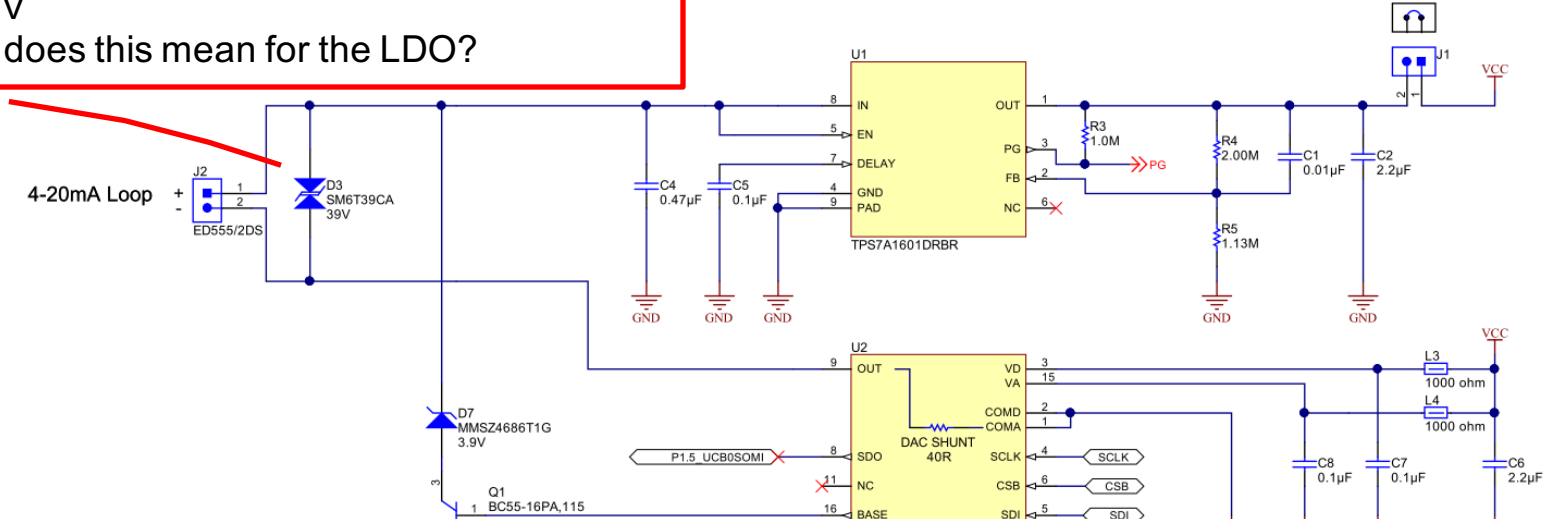- 74.36V
- What does this mean for the LDO?




There is some uncertainty due to the different pulses.



Alternative: SMCJ series

$V_{cl}=58.63V @ 28.2A; 125C; 10/1000\mu s$

 → Package size: $7.9 \times 5.9 = 46.6mm^2$ vs. $19.4mm^2$ (of SMBJ series)



TVS – Layout recommendations

  

- Use 4-terminal connection type to mitigate parasitic inductance effect
- Place TVS on same layer as DUT
- Increase solder pad size to reducing heating of TVS

App Report; Electrical Transient Immunity
for Power-Over-Ethernet; [slva233a](#)

Agenda

- Introduction to IEC61000-4 EMC Immunity Test Suite
- Surge Protection with TVS Diode and implications for the system
- Example Implementation 1: Loop-powered 4-20mA Transmitter
 - Surge Protection
 - Reverse Polarity Protection
 - Current LimitingExamples: TIDA-00167, TIDA-00648, TIDA-00165, TIDA-00189
- Example implementation 2: Combined Voltage / Current output


TVS usage – a real example

2-wire loop powered 4-20mA interface

Surge
1kV, DM, 42Ω
TA ~125°C

Q2 / Q3, NPN BJT
VCEO = 80 / 60V

U1, LDO
abs max VIN=62V

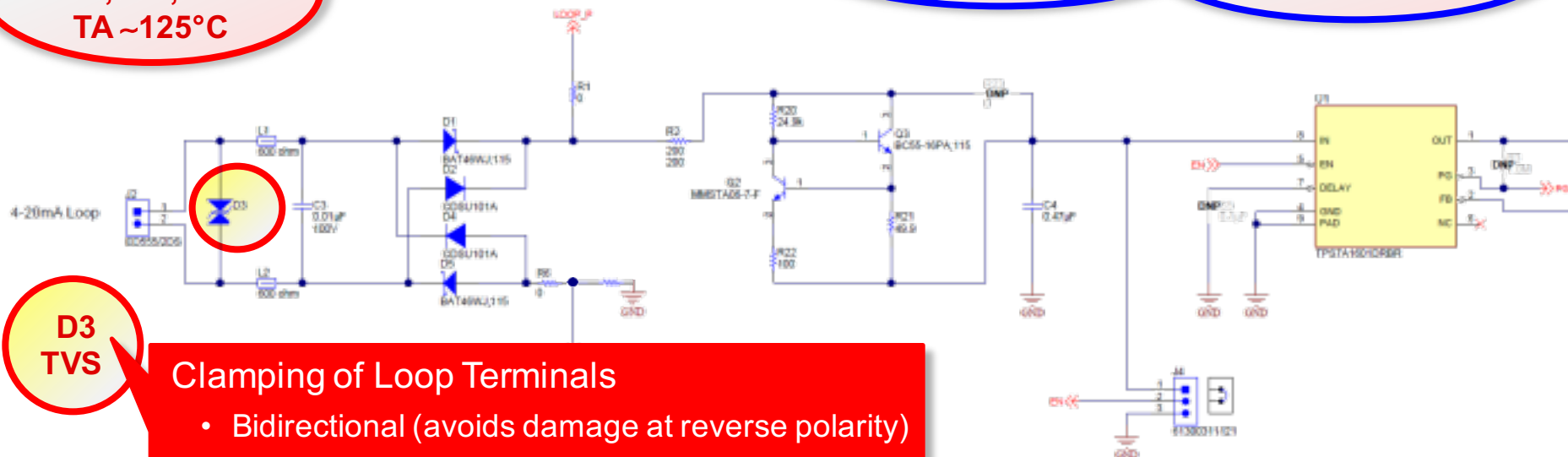


2-wire loop powered 4-20mA interface

Reverse Polarity Protection

D1 / D5, Schottky
VR = 100V, VF
D2 / D4, Si –Diodes
VR = 80V, low leakage



Reverse Polarity Protection

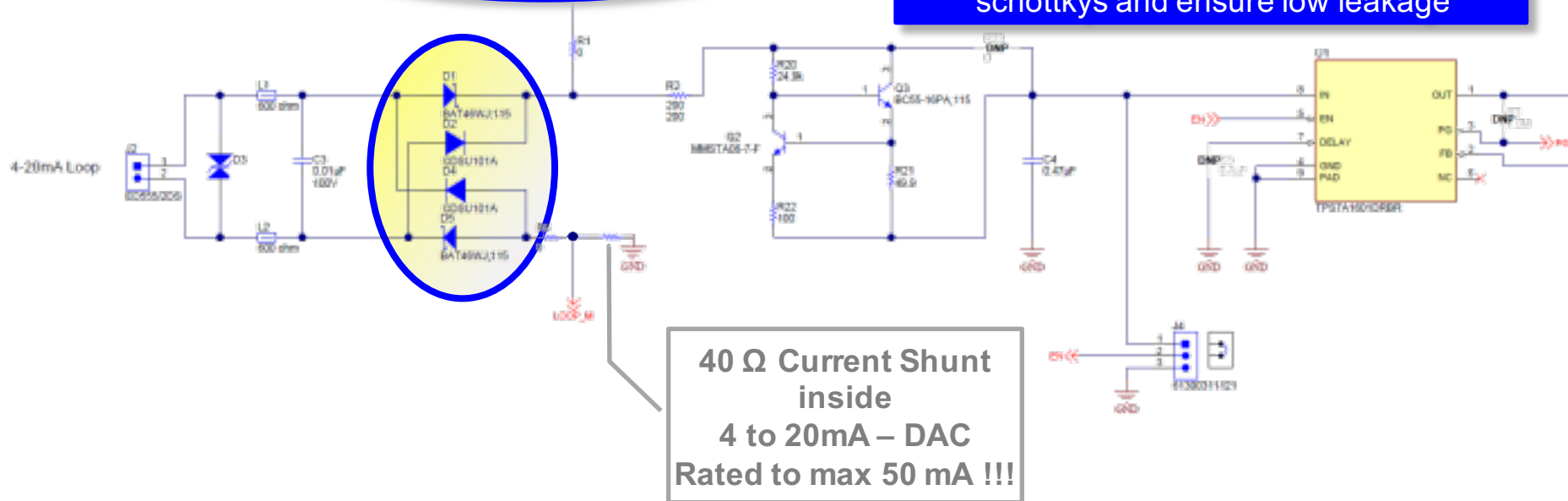- Schottkys ensure low voltage losses
- Si-Diodes clamp reverse voltage of schottkys and ensure low leakage



Reverse Polarity Protection – Different Approaches (I)



Half-Wave Rectification (Single Diode)

 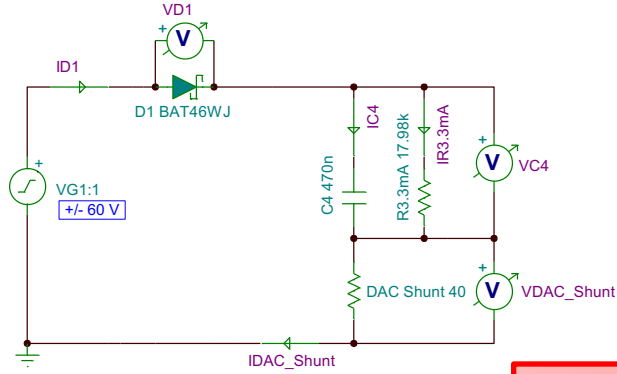

VR > 2 x VG

VR > VG
???

Half-Wave Rectification (Dual Diode)

 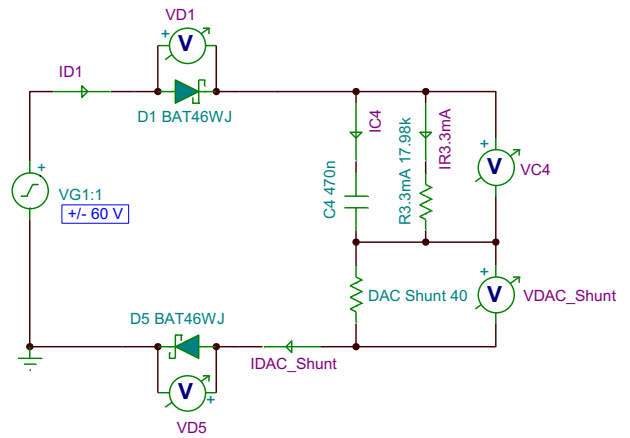

-59.7 V for VD1 & VD5 ???

2-wire loop powered 4-20mA interface

Reverse Polarity Protection – Different Approaches (II)

- Reverse leakage of diodes shows large variations, b/w typ and max values
- Min values not even given

I_R reverse current

Conditions


$V_R = 75\text{ V}$

$V_R = 75\text{ V}; T_j = 60\text{ }^\circ\text{C}$

| Min | Typ | Max | Unit |
|-----|-----|-----|---------------|
| - | 1 | 4 | μA |
| - | - | 80 | μA |

- Increased Leakage of D5 simulated by paralleling R1

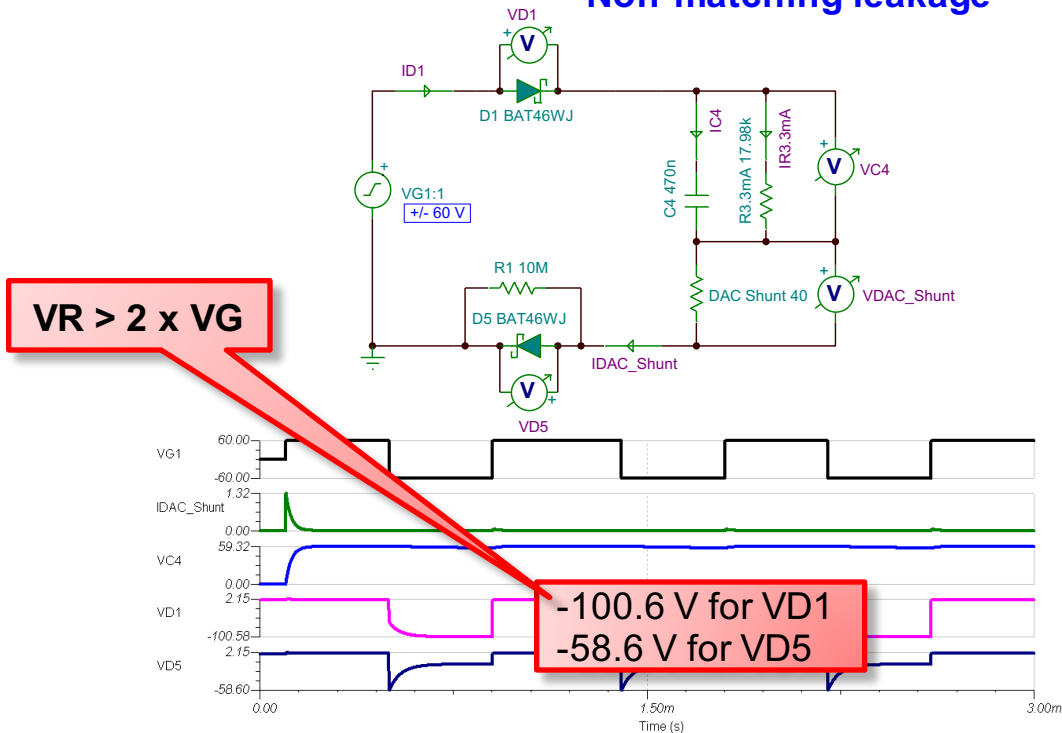
Half-Wave Rectification (Dual Diode) Non-matching leakage



Reverse Polarity Protection – Different Approaches (III)


Non-matching leakage

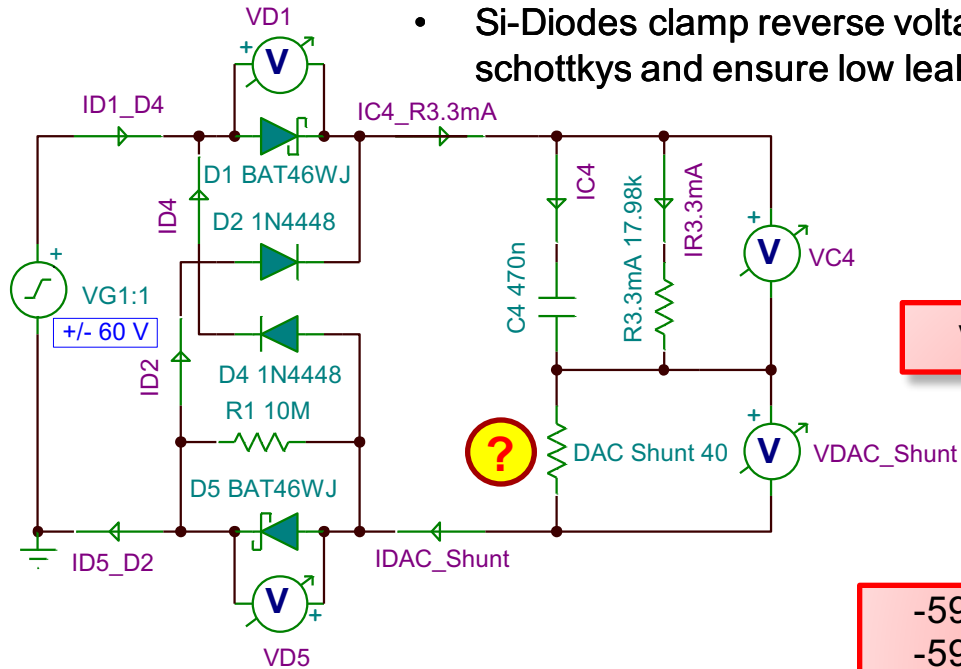- Schottkys ensure low voltage losses
- Si-Diodes clamp reverse voltage of schottkys and ensure low leakage



VR > VG

-59.8 V for VD1
-59.6 V for VD5


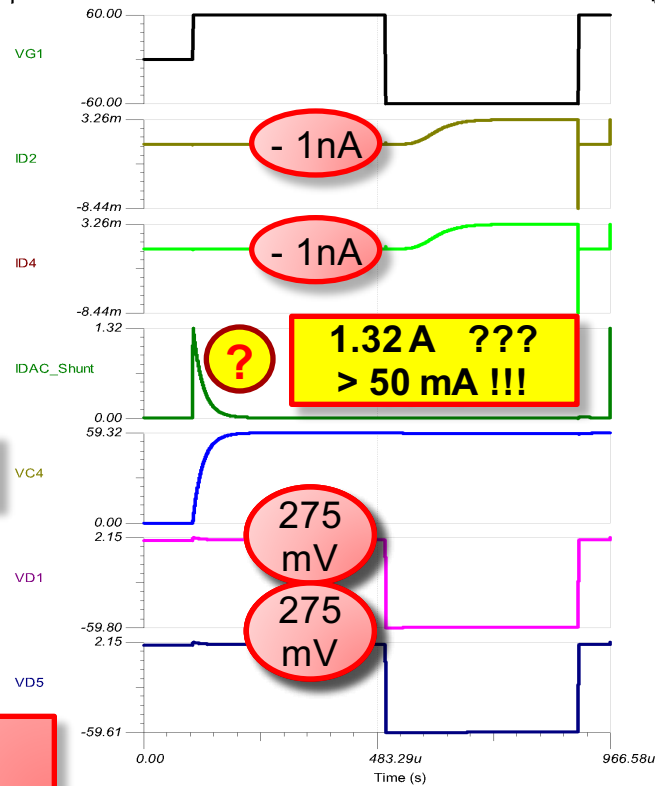


2-wire loop powered 4-20mA interface



Current Limiting – Different Approaches (I)

- Reduces Current Surge through the DAC's internal 40 Ω Current Shunt During Hot Plug and Positive Surge

200 Ω Current Limiting Resistor

 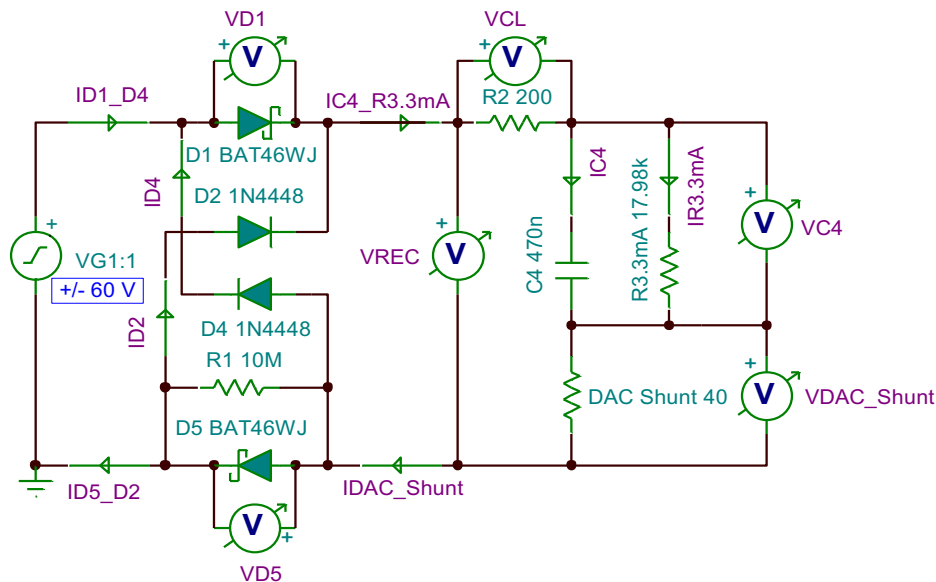


A Simple Active Current Limiter

 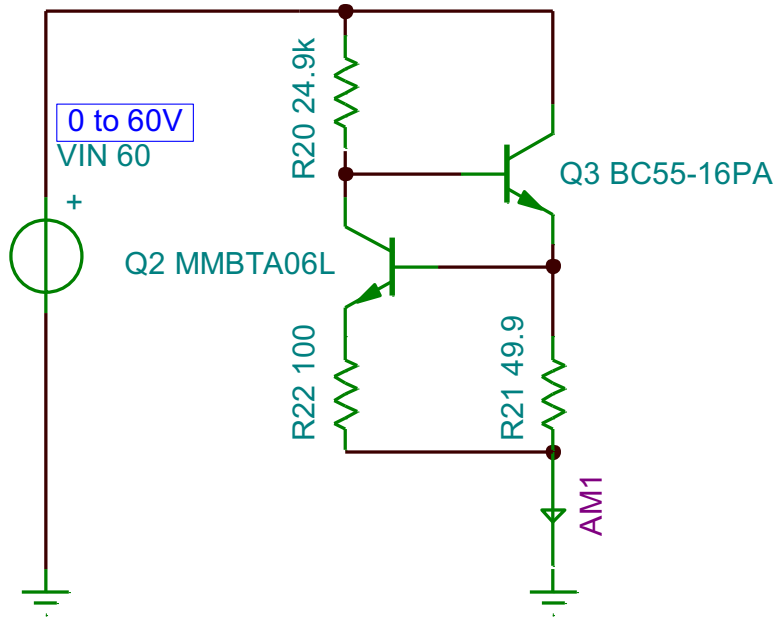


2-wire loop powered 4-20mA interface

Current Limiting – Different Approaches (II)

Active Current Limiter

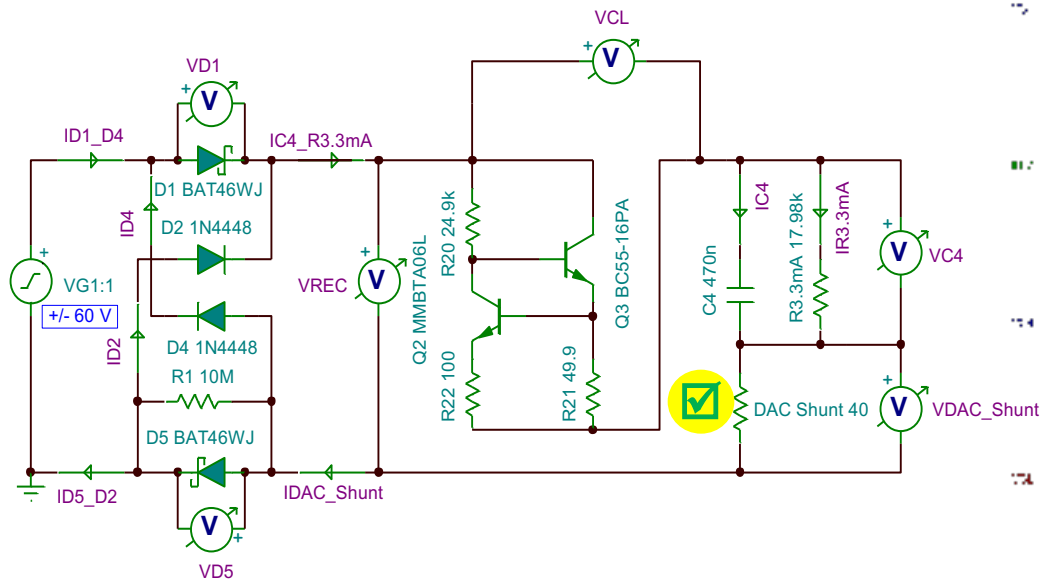

 
- For 1.33V drop @ 3.34mA (nominal operation) a 390 Ω current limiting resistor would be needed
- **Max IDAC_Shunt: $\sim 59.5 \text{ V} / (390 \Omega + 40 \Omega) \sim 140 \text{ mA} !!$**




Agenda

- Introduction to IEC61000-4 EMC Immunity Test Suite
 - Surge Protection with TVS Diode and implications for the system
 - Example Implementation 1: Loop-powered 4-20mA Transmitter
 - Example implementation 2: Combined Voltage / Current output
 - Surge Protection
 - TVS Diodes
 - Current Steering Diodes + Current Limiting Resistors
 - Reverse Polarity Protection
 - Clamping of internal voltage rails
- Example: TIDA-00559

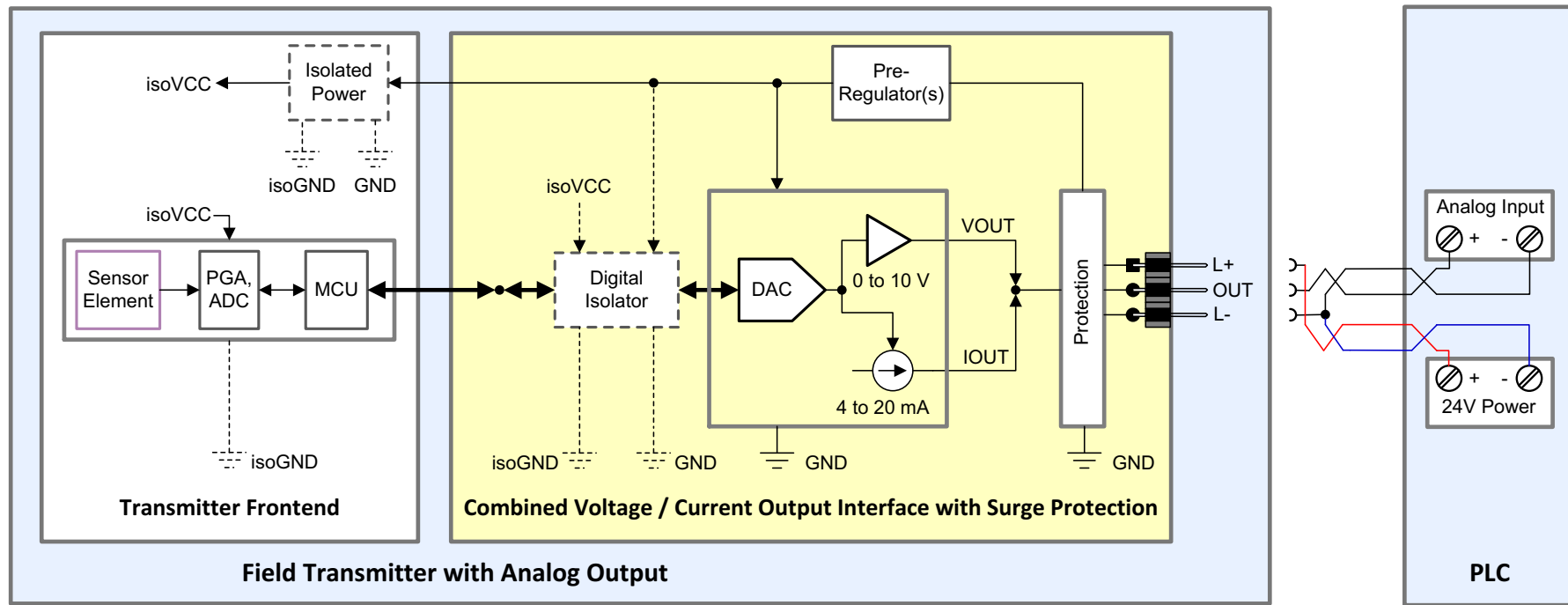TIDA-00559: Combined Voltage / Current Interface Systems View




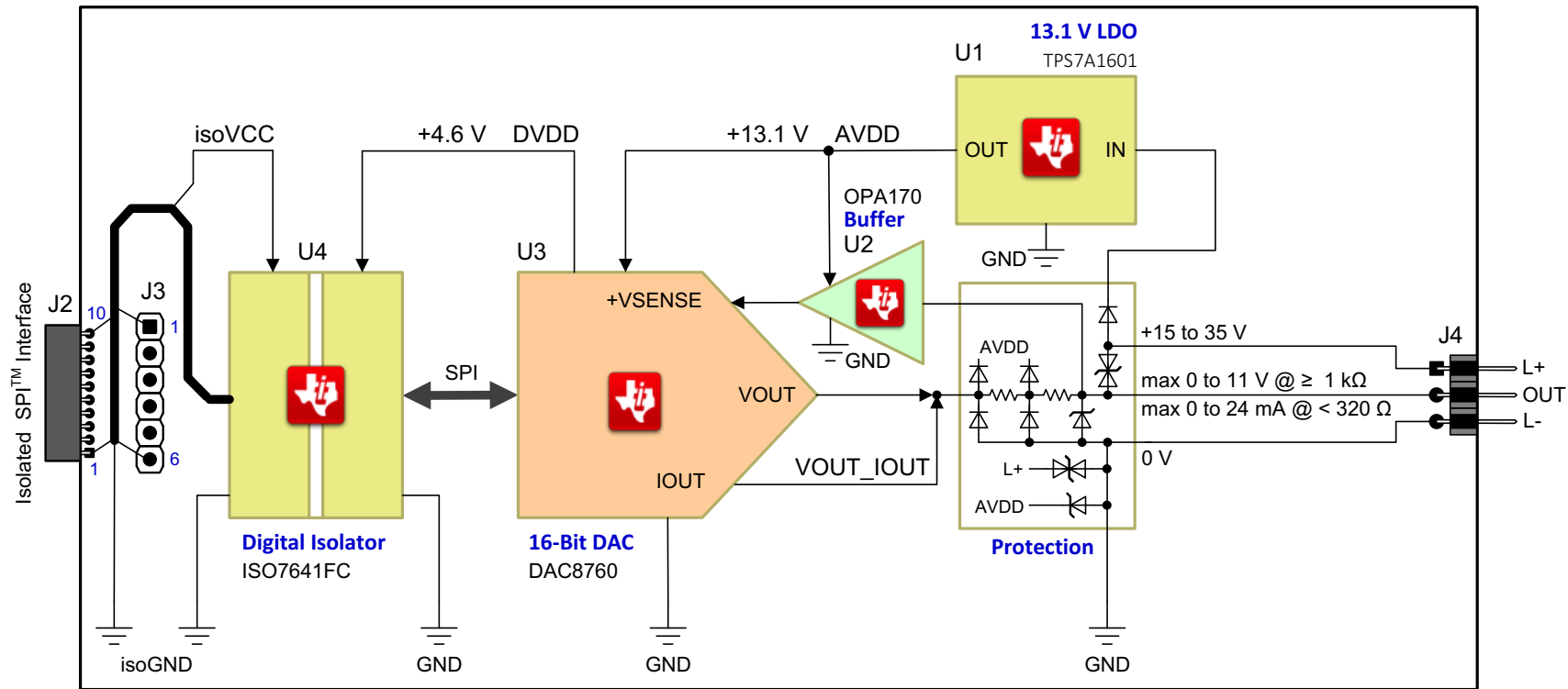TIDA-00559: Combined Voltage / Current Output Detailed Block Diagram




Combined Voltage / Current Output

Basic Protection on Interface Connector

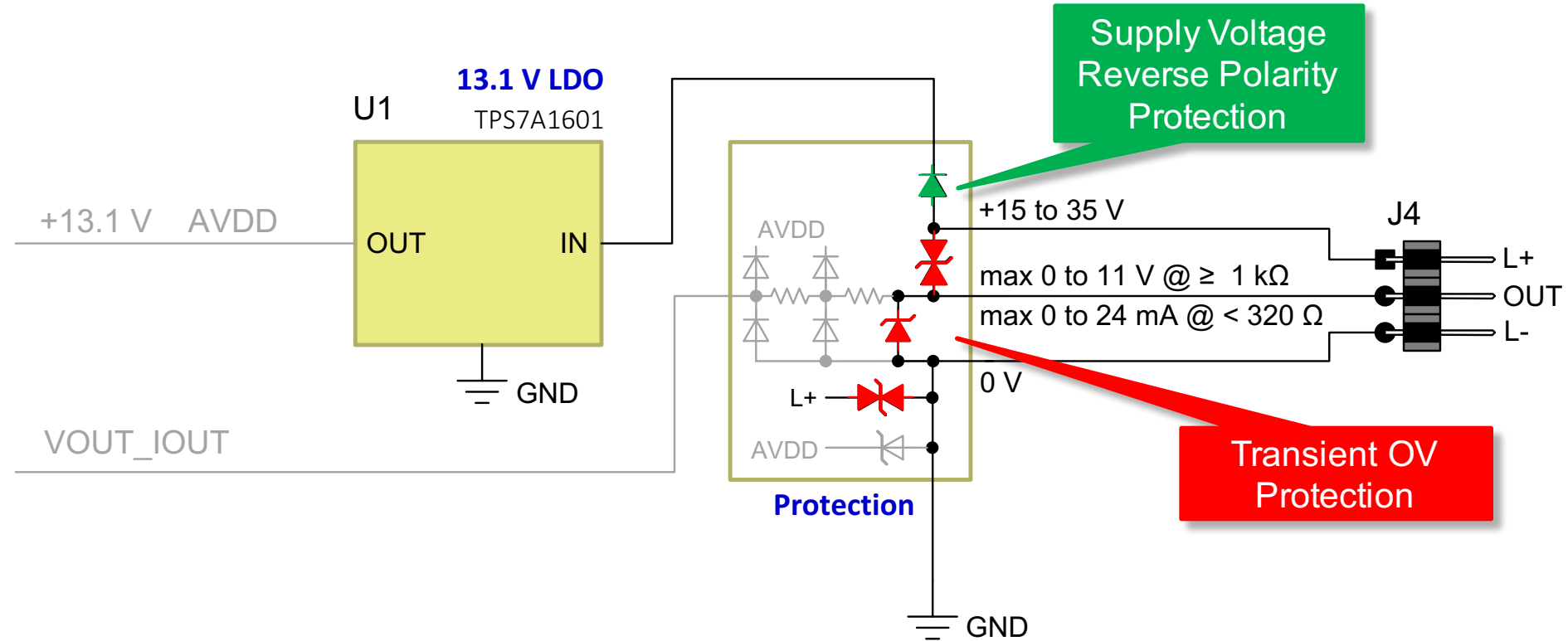

Basic Protection on Interface Connector

Transient OV Protection - Details

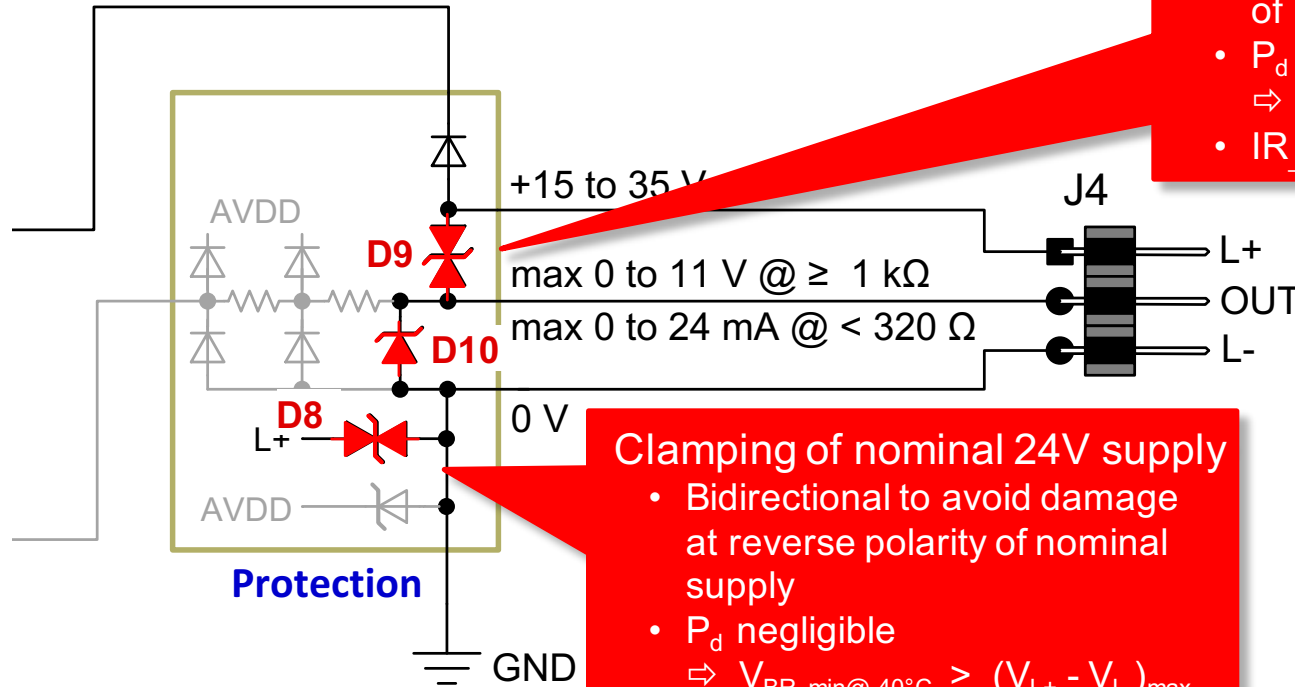

Voltage Clamping b/w L+ and OUT


- Bidirectional to avoid damage of D9 and D10 at reverse polarity of nominal supply
- P_d negligible
 $\Rightarrow V_{BR_min@-40^\circ\text{C}} > 35 \text{ V}$
- $IR_{_max@+85^\circ\text{C}, 35\text{V}} < 1 \mu\text{A}$

Clamping of nominal 24V supply

- Bidirectional to avoid damage at reverse polarity of nominal supply
- P_d negligible
 $\Rightarrow V_{BR_min@-40^\circ\text{C}} > (V_{L+} - V_{L-})_{\text{max}}$
- $V_{CL_max@+100^\circ\text{C}} < VIN_{\text{max_U1}}$

Basic Protection on Interface Connector

Transient OV Protection - Details

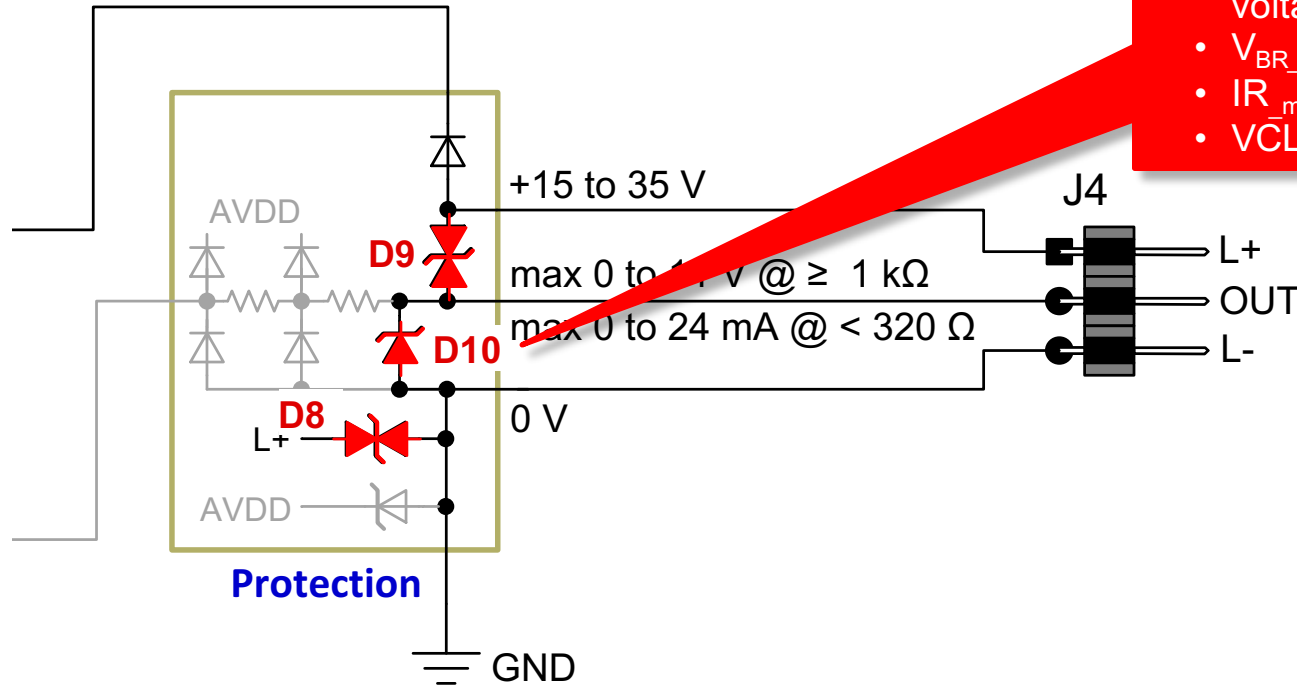


Voltage Clamping b/w OUT and L-

- Unidirectional fits best the unipolar voltage range on OUT
- $V_{BR_min@-40^{\circ}\text{C}} > AVDD$
- $I_{R_max@+85^{\circ}\text{C}, 7.7\text{V}} < 1 \mu\text{A}$
- $V_{CL_max@+125^{\circ}\text{C}} < AVDD$

Protection of output pins of the 16-Bit DAC

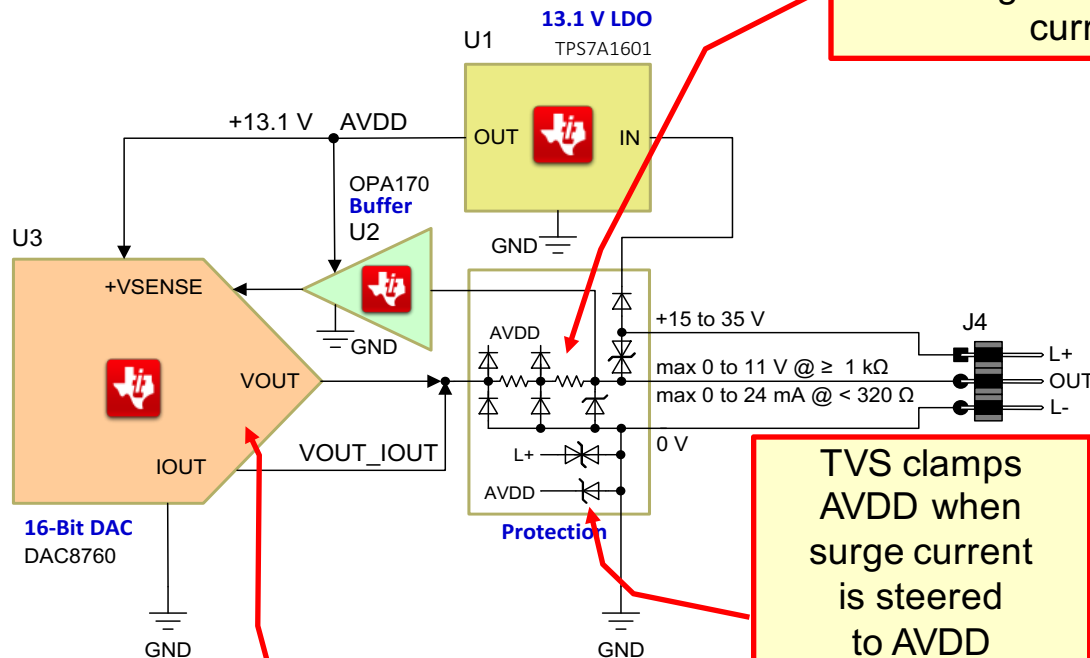
Steering diodes steer current to AVDD or GND, current is limited by resistors



TVS clamps AVDD when surge current is steered to AVDD

Voltages on IOU_T & VO_U_T must not exceed AVDD nor go below GND or current needs to be limited

The real circuit DAC

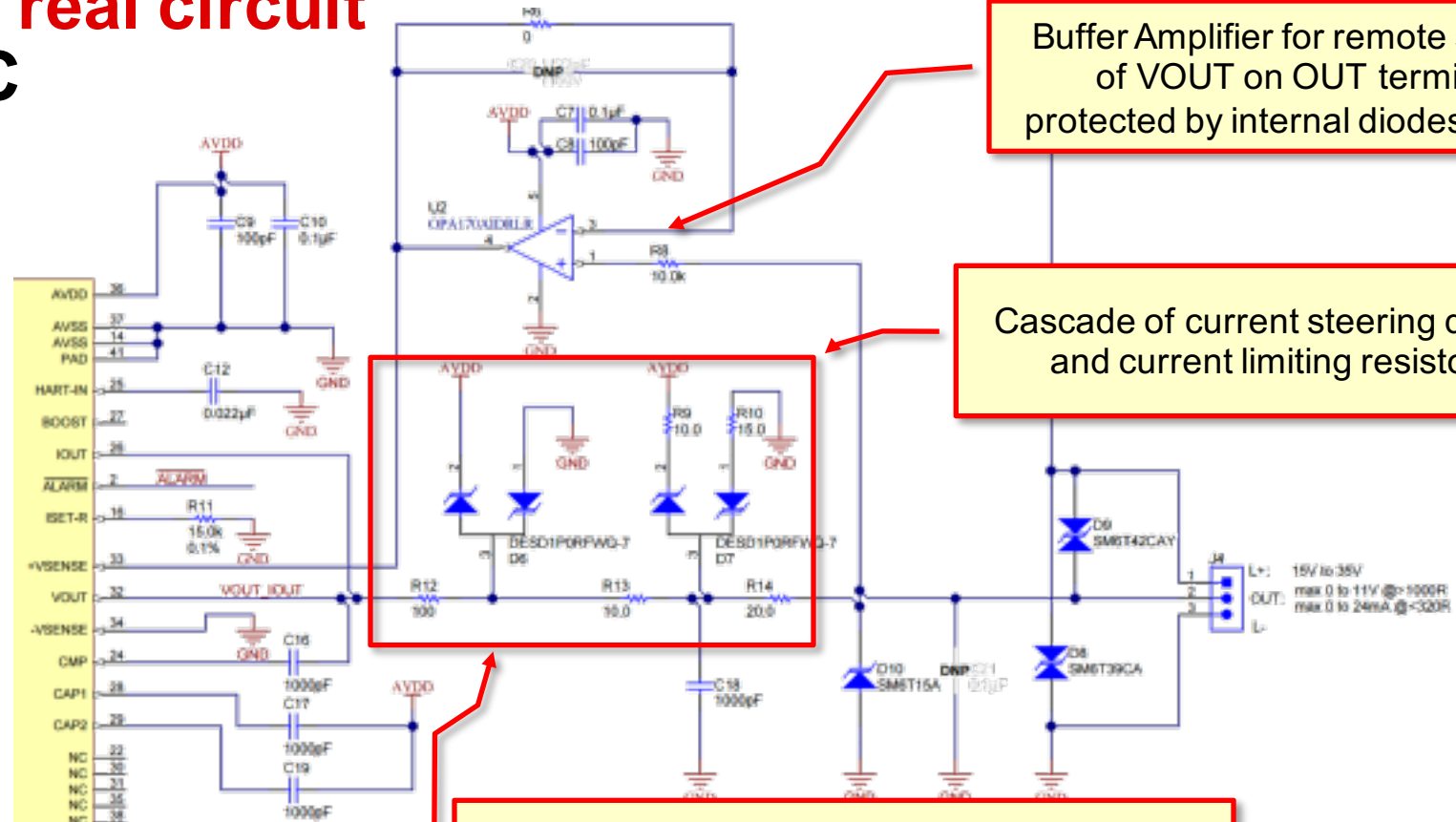

Buffer Amplifier for remote sensing of VOUT on OUT terminal, protected by internal diodes and R8

Cascade of current steering diodes and current limiting resistors

Resistors limit current, but cause voltage drop:
VOUT mode: $130\ \Omega \times 11\text{mA} = 1.43\text{V}$
IOUT mode: $130\ \Omega \times 24\text{mA} = 3.12\text{V}$

Effects of current limiting resistors:

How to deal with the voltage drops ?

- **VOUT mode:**

- Buffer Amplifier for remote sensing compensates for voltage drops
- Need for increased footroom when sinking current into VOUT
 - Can be addressed by bipolar supply of DAC

- **IOUT mode:**

- Worst case drop of 3.12V reduces significantly the maximum achievable output voltage and therefore the maximum usable load resistance in the loop:

| | | | |
|------------|---------|---------------------------------|---------------|
| • AVDDtyp: | 13.12 V | AVDD_min: | 12.84 V |
| | | - VCOMPLIANCE_max | 2.00 V |
| | | - <u>VDROP on c/l resistors</u> | <u>3.12 V</u> |
| | | VOUT_max on J4 | <u>7.72 V</u> |

- $R_{LOAD_max} = V_{OUT_max} \text{ on J4} / I_{OUT_max} = 7.72V / 24 \text{ mA} = \underline{\underline{321.7 \Omega}}$


The real circuit

LDO

TVS clamps AVDD when surge current is steered to AVDD



Protects LDO's internal FET when not powered, but surge is applied b/w OUT and L- of J4

Reverse Input protection for LDO

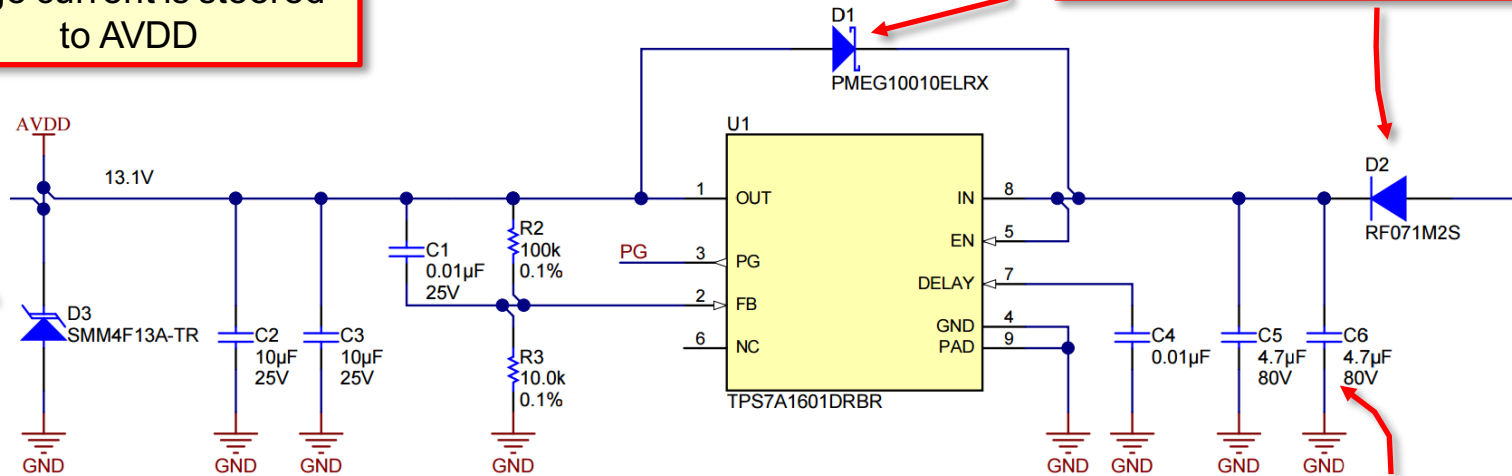

LDO Input Bypass Caps, Stored energy avoids System Reset during negative surge

Layout Example TIDA-00559

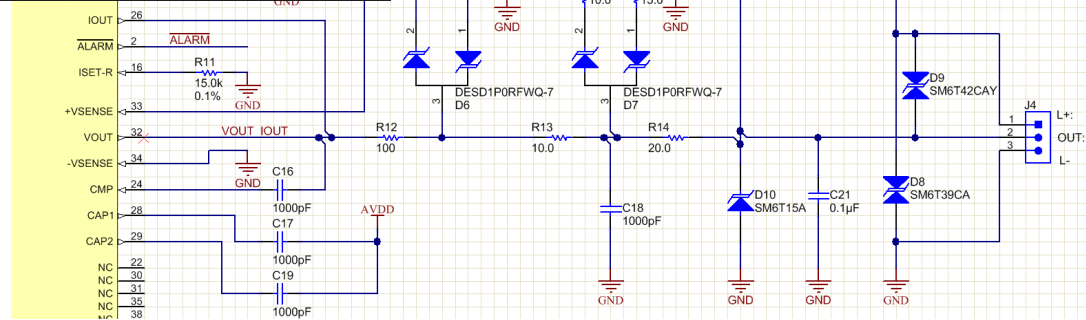 

Conclusion

- Introduction to IEC61000-4 EMC Immunity Test Suite
 - Surge Immunity test is the most severe.
 - TVS diode as countermeasure
- Surge Protection with TVS Diode and implications for the system
 - Understanding of TVS parameters and characteristic
 - Selection process of TVS
- Example Implementations:
 - Loop-powered 4-20mA Transmitter
 - Combined Voltage / Current output
 - Practical protection circuits and their side effects

Thank You!

Questions?